

Introduction to Electrical Engineering Practice Exam

Discussion: January 12, 2026

1 Conceptual Understanding: Multiple Choice

Select exactly one answer per question.

Fundamentals

1. The drift motion of electrons in a conductor is mainly caused by:

- A) temperature gradients
- B) magnetic fields
- C) the electric field
- D) mechanical forces

Solution: C

2. For a metallic conductor, an increase in temperature usually leads to:

- A) decreasing resistance
- B) sudden insulating behavior
- C) unchanged resistance
- D) increasing resistance

Solution: D

DC

3. Kirchhoff's current law states:

- A) The sum of voltages in a loop is zero.
- B) The sum of currents at a node is zero.
- C) The sum of resistances at a node is constant.
- D) Power is stored at a node.

Solution: B

4. An ideal voltage source is characterized by:

- A) a fixed voltage independent of current

- B) a fixed current independent of the load
- C) infinite internal resistance
- D) no influence on connected circuits

Solution: A

5. The nodal-voltage method primarily works with:

- A) mesh currents
- B) node voltages
- C) equivalent sources
- D) frequency analysis

Solution: B

6. For maximum power transfer from a source to a purely resistive load:

- A) load resistance $\gg$ source resistance
- B) load resistance $\ll$ source resistance
- C) load resistance equals source internal resistance
- D) load resistance equals zero

Solution: C

7. An ammeter is typically connected:

- A) in parallel with the measured quantity
- B) in series with the measured quantity
- C) with zero internal resistance
- D) only in AC circuits

Solution: B

Fields & Components

8. A capacitor primarily stores:

- A) magnetic energy
- B) mechanical energy
- C) thermal energy
- D) electric energy

Solution: D

9. Under constant DC voltage, a capacitor behaves (in steady state) like:

- A) a short circuit
- B) an open circuit (no current flow)
- C) a resistor with fixed value
- D) a voltage source

Solution: B

10. Magnetic fields are mainly generated by:

- A) stationary charges
- B) moving charges or electric current
- C) temperature changes
- D) light radiation

Solution: B

11. Electrical induction occurs when:

- A) the voltage remains constant
- B) the conductor length remains constant
- C) the magnetic flux through an area changes
- D) no charges are present

Solution: C

12. An inductor opposes rapid changes in current because it:

- A) stores electric energy
- B) stores magnetic energy
- C) generates heat
- D) neutralizes charges

Solution: B

13. An ideal transformer can:

- A) convert DC voltage to higher DC voltage
- B) convert AC voltage to AC voltage with different amplitude
- C) permanently change the frequency of AC voltage
- D) generate energy

Solution: B

14. A transient process in an electrical network refers to:

- A) an instantaneous change without time dependence
- B) a time-dependent transition toward steady state
- C) a permanent state without variation
- D) a purely mathematical concept without physical meaning

Solution: B

AC

15. A phasor represents:

- A) the complete time-domain waveform
- B) DC quantities only
- C) only the real part of a quantity
- D) a complex amplitude (magnitude and phase) at fixed frequency

Solution: D

16. The reactance of a capacitor decreases with increasing frequency:

- A) increases
- B) decreases
- C) remains constant
- D) is unpredictable

Solution: B

17. Reactive power occurs in an AC circuit when:

- A) voltage and current are phase-shifted
- B) voltage and current are exactly in phase
- C) no energy is transferred
- D) only DC current flows

Solution: A

18. A high-pass filter ideally allows:

- A) low frequencies
- B) no signals
- C) DC only
- D) high frequencies

Solution: D

19. Resonance in a resonant circuit typically means:

- A) minimum impedance / maximum current (series circuit)
- B) maximum damping
- C) no load influence
- D) instantaneous decay

Solution: A

20. A practical advantage of a symmetrical three-phase system is:


- A) lower frequency
- B) only two conductors are required
- C) generation of a rotating magnetic field (e.g. for motors)
- D) no balancing current possible

Solution: C

2 DC Networks

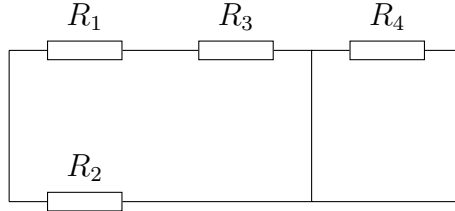2.1 Equivalent Resistance

Given the resistor network with $R_1 = 10\ \Omega$, $R_2 = 20\ \Omega$, $R_3 = 30\ \Omega$, $R_4 = 15\ \Omega$:



Calculate the equivalent resistance of the network.

Solution:


$$R_{12} = \frac{R_1 R_2}{R_1 + R_2} = \frac{10 \cdot 20}{30} = 6.67\ \Omega$$

$$R_{123} = 6.67 + 30 = 36.67\ \Omega$$

$$R = \frac{36.67 \cdot 15}{36.67 + 15} \approx 10.7\ \Omega$$

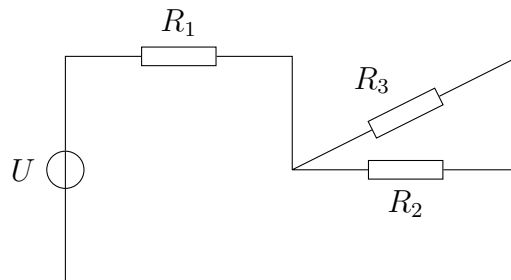2.2 Network Analysis

Given the circuit with $R_1 = 6\ \Omega$, $R_2 = 12\ \Omega$, $R_3 = 4\ \Omega$ and a voltage source of $24\ \text{V}$:



Determine:

1. the total source current,
2. the branch currents through R_2 and R_3 ,
3. the power dissipated in R_3 .

Solution:

$$R_{23} = \frac{12 \cdot 4}{16} = 3\ \Omega$$

$$R = 6 + 3 = 9\ \Omega$$

$$I = \frac{24}{9} = 2.67\ \text{A}$$


$$U_{23} = I \cdot 3 = 8\ \text{V}$$

$$I_2 = \frac{8}{12} = 0.67\ \text{A}, \quad I_3 = \frac{8}{4} = 2\ \text{A}$$

$$P_3 = I_3^2 R_3 = 16\ \text{W}$$

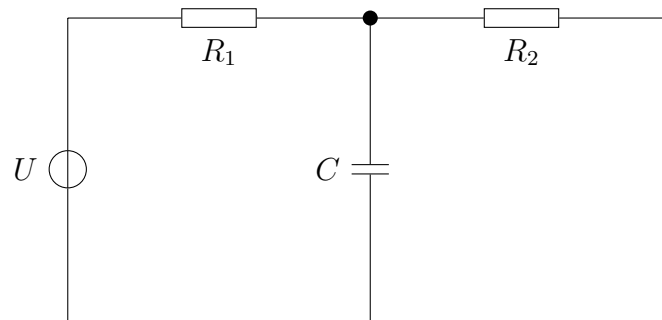2.3 Nodal Analysis

Given the DC network with $U = 20\text{ V}$, $R_1 = 5\ \Omega$, $R_2 = 10\ \Omega$, $C = 100\ \mu\text{F}$:



The lower conductor is chosen as reference potential (ground). The steady-state condition ($t \rightarrow \infty$) is assumed.

Determine:

1. the node voltage at the marked node,
2. the voltage across the capacitor,
3. the current through the capacitor,
4. the energy stored in the capacitor.

Solution:

$$\frac{V_1 - 20}{R_1} + \frac{V_1 - 0}{R_2} = 0$$

$$2(V_1 - 20) + V_1 = 0$$

$$V_1 = \frac{40}{3} \approx 13.33\text{ V}$$

$$U_C = V_1 - 0 = 13.33\text{ V}$$


$$i_C = C \frac{du_C}{dt} = 0$$

$$E = \frac{1}{2} C U_C^2 \approx 8.9\text{ mJ}$$

3 AC Networks

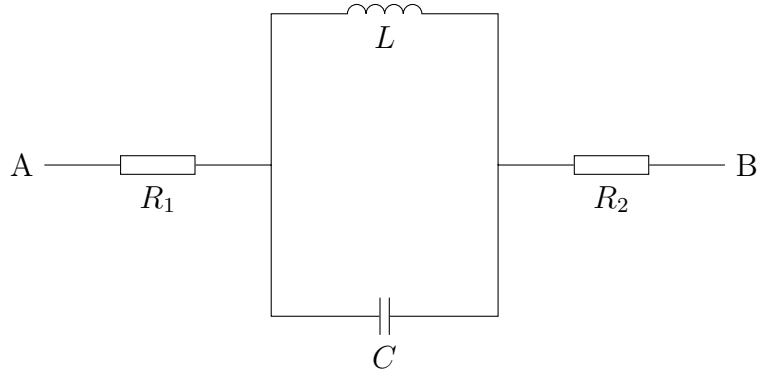3.1 Equivalent Impedance

Given the AC network with $R_1 = 10\ \Omega$, $R_2 = 20\ \Omega$, $L = 50\ \text{mH}$, $C = 100\ \mu\text{F}$, $\omega = 1000\ \text{rad/s}$:



Determine:

1. the complex impedances of the individual components,
2. the complex equivalent impedance between terminals A and B,
3. the magnitude and phase of the equivalent impedance.

Solution:

$$Z_R = R$$

$$Z_L = j\omega L = j \cdot 1000 \cdot 0.05 = j50\ \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 1000 \cdot 100 \cdot 10^{-6}} = -j10\ \Omega$$

$$Z_{LC} = \left(\frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = \frac{1}{j0.08} = -j12.5\ \Omega$$


$$Z = R_1 + Z_{LC} + R_2 = (30 - j12.5)\ \Omega$$

$$|Z_{\text{ges}}| = \sqrt{30^2 + 12.5^2} \approx 32.5\ \Omega$$

$$\varphi = \arctan\left(\frac{-12.5}{30}\right) \approx -22.6^\circ$$

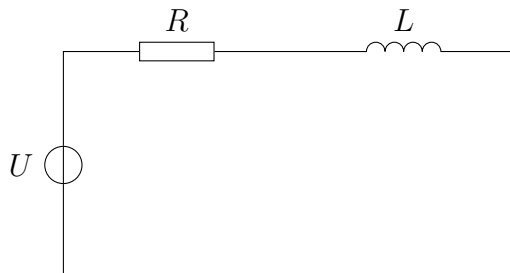3.2 Complex Network Analysis

Given the following network with a sinusoidal voltage source $U = 230\ \text{V}$, $f = 50\ \text{Hz}$ and the components $R = 20\ \Omega$, $L = 100\ \text{mH}$:



Determine:

1. the complex impedance Z ,
2. the RMS current I ,
3. the phase shift between current and voltage,
4. the power factor $\cos \varphi$,
5. the active power P ,
6. the reactive power Q .

Solution:

$$\omega = 2\pi f = 314 \text{ rad/s}$$

$$X_L = \omega L = 31.4 \Omega$$

$$Z = 20 + j31.4 \Rightarrow |Z| = 37.3 \Omega$$

$$I = \frac{230}{37.3} = 6.17 \text{ A}$$

$$\varphi = \arctan\left(\frac{31.4}{20}\right) = 57.5^\circ$$

$$\cos \varphi = 0.54$$

$$P = UI \cos \varphi = 766 \text{ W}$$

$$Q = UI \sin \varphi = 1180 \text{ var}$$