

Select exactly one answer per question.

1. Which quantity is decisive for the thermal load of a current-carrying conductor?

- A) the electric field strength
- B) the electrical power
- C) the electrical current density
- D) the electrical resistance

Solution: C

2. An ideal ohmic resistor is characterized by the fact that

- A) current and voltage are proportional to each other.
- B) a phase shift occurs between current and voltage.
- C) the resistance value is time-dependent.
- D) electrical energy is periodically stored and released.

Solution: A

3. Which statement describes the I – V characteristic of an ideal current source?

- A) The voltage is proportional to the current.
- B) The current is independent of the terminal voltage.
- C) The characteristic passes through the origin.
- D) The characteristic is frequency-dependent.

Solution: B

4. Which statement about electrical power and energy is correct?

- A) Power and energy are independent of each other.
- B) Energy is the time derivative of power.
- C) With constant power, energy increases linearly with time.
- D) Power and energy differ only by a constant factor.

Solution: C

5. Kirchhoff's voltage law is a consequence of:

- A) conservation of charge
- B) conservation of momentum
- C) conservation of temperature
- D) conservation of energy

Solution: D

6. A Y- Δ transformation is permissible in a DC network if
- A) all resistors have the same value.
 - B) the network is supplied by only one voltage source.
 - C) no power is dissipated in the network.
 - D) the current-voltage relationships at the external terminals remain unchanged.

Solution: D

7. Ideally, a voltmeter has:
- A) a small internal resistance
 - B) a large internal resistance
 - C) no internal resistance
 - D) a frequency-dependent resistance

Solution: B

8. Which statement correctly describes the efficiency of an electrical system?
- A) It is the ratio of output power to input power.
 - B) It is the ratio of reactive power to active power.
 - C) It is independent of the electrical losses in the system.
 - D) In AC operation, it can be greater than one.

Solution: A

9. Which statement about electric and magnetic field lines is correct?
- A) Electric field lines are always closed.
 - B) Magnetic field lines are always closed.
 - C) Magnetic field lines end at magnetic charges.
 - D) Electric field lines exist only inside conductors.

Solution: B

10. Which of the following quantities is a directly measurable physical field in macroscopic electrodynamics?
- A) electric displacement **D**
 - B) magnetic field strength **H**
 - C) magnetic flux density **B**
 - D) electric polarization **P**

Solution: C

11. A time-varying magnetic field generates, according to Faraday's law:

- A) an induced voltage
- B) a constant current
- C) heat
- D) a mechanical force

Solution: A

12. Why can the voltage across an ideal capacitor not change abruptly?

- A) Because the capacitor blocks direct current, rapid voltage changes are not possible.
- B) An ideal capacitor fundamentally prevents any change in the stored energy.
- C) An abrupt change in voltage would require an infinitely large current.
- D) The voltage across a capacitor is limited from above by the capacitance.

Solution: C

13. Under constant DC voltage, an ideal inductor in the steady state behaves like:

- A) an open circuit
- B) a current source
- C) a voltage source
- D) a short circuit

Solution: D

14. A capacitor is discharged through an ohmic resistor. Which statement correctly describes the discharge process?

- A) The voltage across the capacitor decreases exponentially, while the current increases exponentially.
- B) The voltage across the capacitor increases exponentially, while the current decreases exponentially.
- C) The voltage across the capacitor decreases exponentially, and the current also decreases exponentially.
- D) The voltage across the capacitor increases exponentially, and the current also increases exponentially.

Solution: C

15. Why is the RMS value typically specified for mains voltages?

- A) Because it is smaller than the peak value.
- B) Because it describes the power effect of the voltage in ohmic loads.
- C) Because it is independent of frequency.
- D) Because it completely describes the time dependence of the voltage.

Solution: B

16. For an ideal inductor in an AC circuit, the following applies:

- A) The current leads the voltage.
- B) The current lags behind the voltage.
- C) Current and voltage are phase-shifted by 45° relative to each other.
- D) Current and voltage are in phase.

Solution: B

17. What physical cause leads to the current leading the voltage in a capacitor?

- A) The voltage causes an immediate current flow through the dielectric.
- B) The voltage is delayed by ohmic losses in the capacitor.
- C) Magnetic effects determine the behavior of the capacitor.
- D) The current charges the capacitor, causing the voltage to build up with a delay.

Solution: D

18. What physical cause leads to the occurrence of reactive power in an AC circuit?

- A) Electrical energy is periodically stored in fields and released again.
- B) Electrical energy is periodically stored in heat and released again.
- C) Electrical energy is periodically returned to the source and stored.
- D) Electrical energy is periodically transported in the conductor and delayed.

Solution: A

19. What filter characteristic is exhibited by a parallel connection of an inductor and a capacitor when it is connected in series with a load?

- A) Low-pass
- B) High-pass
- C) Band-pass
- D) Band-stop

Solution: D

20. A symmetrical three-phase system:

- A) generates a rotating electric field
- B) requires a neutral conductor only with an unbalanced load
- C) operates with direct current
- D) has no voltage between the line conductors

Solution: B